

Norton's Theorem and Maximum Power Transfer

1. Norton's Theorem

Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N , where I_N is the short-circuit current through the terminals and R_N is the input or equivalent resistance at the terminals when the independent sources are turned off.

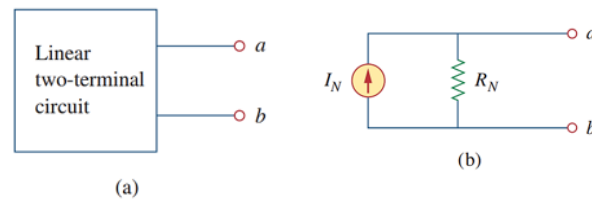


Figure (1) : (a) Original circuit, (b) Norton equivalent circuit.

To find the Norton current I_N , we determine the short-circuit current flowing from terminal a to b in both circuits in Fig.(1). It is evident that the short-circuit current in Fig. (1) (b) is I_N . This must be the same short-circuit current from terminal a to b in Fig. (1)(a), since the two circuits are equivalent. Thus,

$$I_N = i_{sc}$$

Observe the close relationship between Norton's and Thevenin's theorems: $R_N = R_{Th}$, and

$R_N = R_{Th}$	$I_N = \frac{V_{Th}}{R_{Th}}$
----------------	-------------------------------

To determine the Thevenin or Norton equivalent circuit requires that we find:

- The open-circuit voltage v_{oc} across terminals a and b .
- The short-circuit current i_{sc} at terminals a and b .
- The equivalent or input resistance R_{in} at terminals a and b when all independent sources are turned off.

$$V_{Th} = v_{oc}$$

$$I_N = i_{sc}$$

$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$

Example (1): Find the Norton equivalent circuit of the circuit in Fig. (2), at terminals a - b .

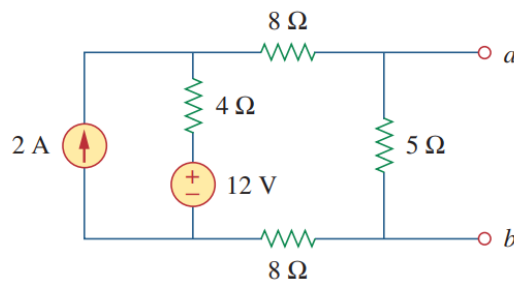


Figure:(2)

Solution:

$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$

$$i_1 = 2 \text{ A}, \quad 20i_2 - 4i_1 - 12 = 0$$

From these equations, we obtain

$$i_2 = 1 \text{ A} = i_{sc} = I_N$$

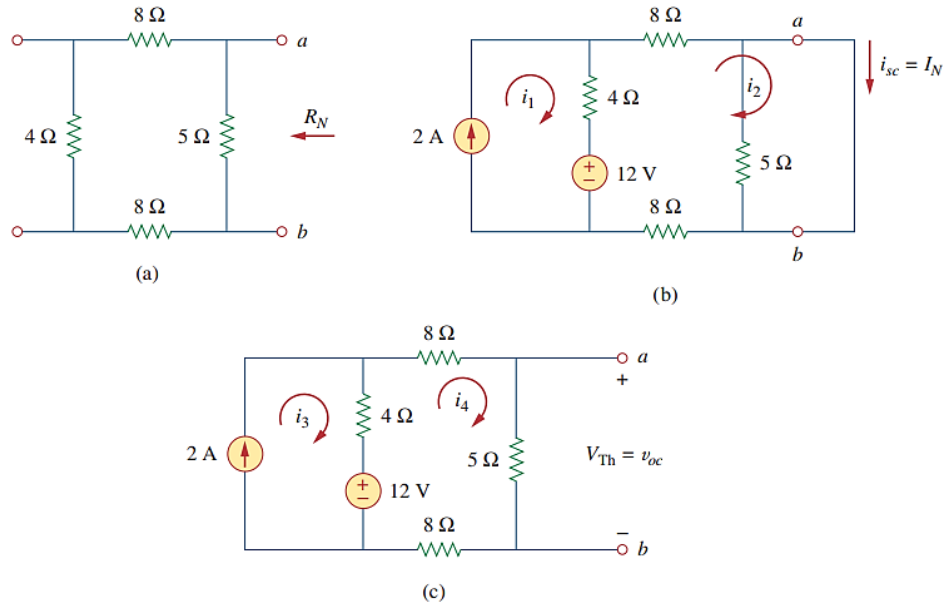


Figure: (3)

$$i_3 = 2 \text{ A}$$

$$25i_4 - 4i_3 - 12 = 0 \quad \Rightarrow \quad i_4 = 0.8 \text{ A}$$

and

$$v_{oc} = V_{Th} = 5i_4 = 4 \text{ V}$$

Hence,

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{4}{4} = 1 \text{ A}$$

Example (2) : Using Norton's theorem, find R_N and I_N of the circuit in Fig. (4) at terminals a-b.

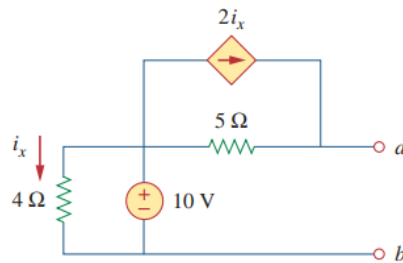


Figure:(4)

$$i_x = \frac{10}{4} = 2.5 \text{ A}$$

$$R_N = \frac{v_o}{i_o} = \frac{1}{0.2} = 5 \Omega$$

At node a, KCL gives

$$i_{sc} = \frac{10}{5} + 2i_x = 2 + 2(2.5) = 7 \text{ A}$$

Thus,

$$I_N = 7 \text{ A}$$

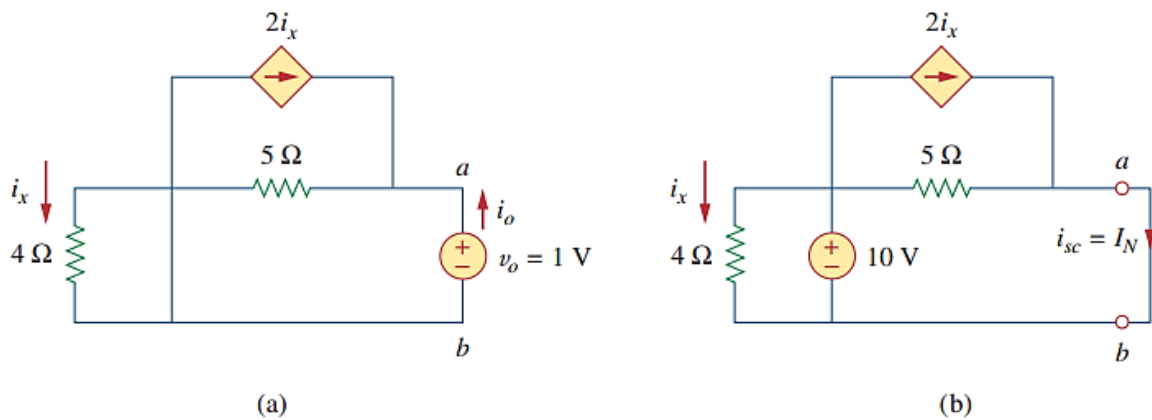


Figure:(5)

2. Maximum Power Transfer

Maximum power is transferred to the load when the load resistance equals the Thevenin resistance as seen from the load ($R_L = R_{Th}$).

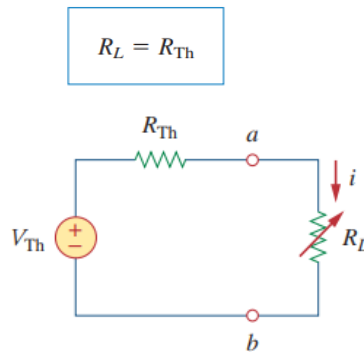


Figure (6): The circuit used for maximum power transfer.

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \dots\dots\dots (1)$$

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}} \dots\dots\dots(2)$$

Example (3): Find the value of R_L for maximum power transfer in the circuit of Fig. (7). Find the maximum power.


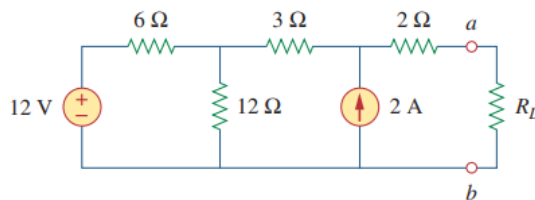


Figure:(7)

Solution :
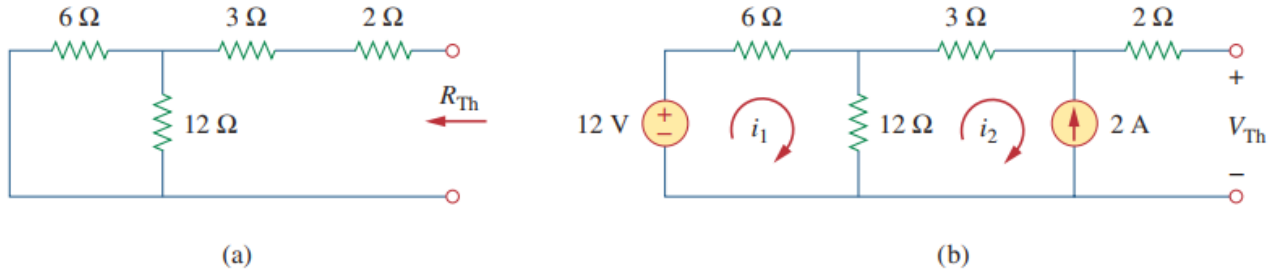
$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$



Figure(8): (a) finding R_{Th} , (b) finding V_{Th} .

$$-12 + 18i_1 - 12i_2 = 0, \quad i_2 = -2 \text{ A}$$

Solving for i_1 , we get $i_1 = -2/3$. Applying KVL around the outer loop to get V_{Th} across terminals $a-b$, we obtain

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0 \quad \Rightarrow \quad V_{Th} = 22 \text{ V}$$

For maximum power transfer,


$$R_L = R_{Th} = 9 \Omega$$

and the maximum power is

$$p_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$


Problems

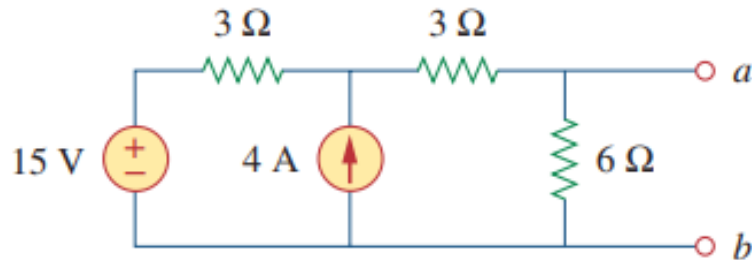1. Find the Norton equivalent circuit for the circuit in Figure below at terminals a-b.




Answer: $R_N = 3 \Omega$, $I_N = 4.5 \text{ A}$.

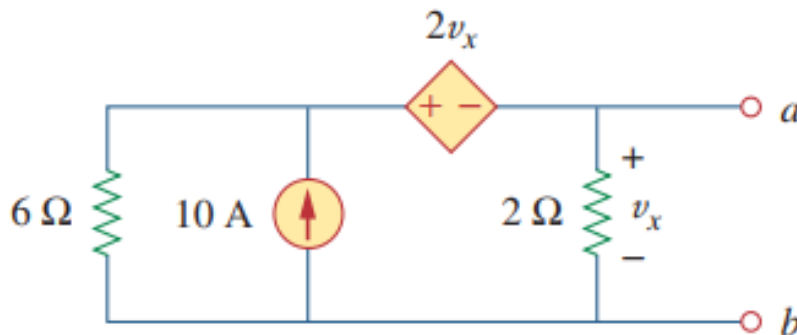2. Find the Norton equivalent circuit of the circuit in Figure below at terminals a-b



Answer: $R_N = 1 \Omega$, $I_N = 10 \text{ A}$.

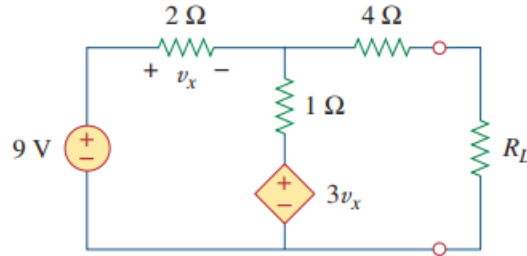3. Determine the value of R_L that will draw the maximum power from the rest of the circuit in Figure below. Calculate the maximum power.



Answer: 4.222 Ω , 2.901 W.